

# Analog VLSI Circuits (AVM 613) - Assignment Report

Rahul Kumar Sinha (SC22B109)  
Indian Institute of Space Science and Technology

October 2025

## 1 Question 1: PMOS Basic Current Mirror Design and Analysis

### 1.1 Problem Statement

A reference current source of  $10\ \mu\text{A}$  is provided. The objective is to design a PMOS current mirror that sources an output current of  $100\ \mu\text{A}$  from  $V_{DD}$ . The current mirror must operate as a current source while the output node voltage ( $V_{OUT}$ ) varies from 0 to  $V_{DD}$ . The tasks include:

- Designing a suitable PMOS current mirror.
- Plotting output current versus  $V_{OUT}$ .
- Determining the maximum permissible  $V_{OUT}$  for current source operation.
- Estimating output impedance ( $R_{OUT}$ ).
- Suggesting a modification (without using cascode) to increase  $R_{OUT}$ .
- Comparing current variation and impedance before and after modification.

### 1.2 Part 1: Basic PMOS Current Mirror (Circuit 1a)

#### 1.2.1 Design and Schematic

The basic PMOS current mirror is designed to source current from  $V_{DD}$  using the relation:

$$\frac{I_{OUT}}{I_{REF}} = \frac{(W/L)_{PM1}}{(W/L)_{PM0}} = 10$$

The design parameters are summarized below:

Table 1: Device Dimensions for Circuit 1a

Parameter	PM0 (Reference)	PM1 (Output)
$W$	$1\ \mu\text{m}$	$10\ \mu\text{m}$
$L$	$100\ \text{nm}$	$100\ \text{nm}$
$W/L$	10	100
$I_{REF}$	$10\ \mu\text{A}$	Target = $100\ \mu\text{A}$

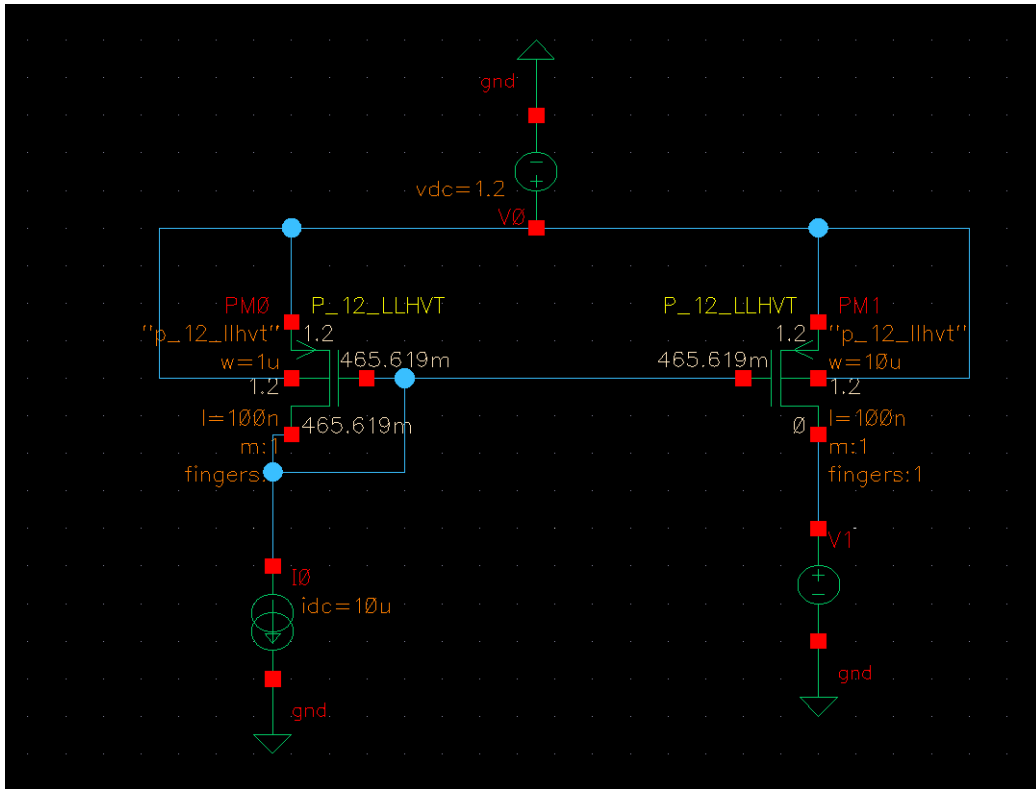


Figure 1: Schematic of the Basic PMOS Current Mirror (Circuit 1a).

### 1.2.2 Simulation Results and Analysis

The DC sweep of  $V_{OUT}$  (from 0 to  $V_{DD}$ ) yields the output current and output impedance plots shown in Figure 2.

 


Figure 2: DC Response of Basic PMOS Current Mirror (Circuit 1a). Red:  $|I_{PM1}|$  ( $\mu A$ ), Blue:  $|R_{OUT}|$  ( $k\Omega$ ).

**Key observations:**

1. **Saturation Region:** The current mirror remains in saturation until approximately  $V_{OUT} = 0.7\text{ V}$ , beyond which *PM1* enters the linear region.

2. **Output Impedance:**

$$R_{OUT} = \frac{1}{\frac{dI_D}{dV_{DS}}} = \frac{1}{g_{ds}}$$

From the plot:

$$R_{OUT,1a} \approx 28.75\text{ k}\Omega$$

3. **Current Variation:**

$$\% \Delta I = \frac{I_{max} - I_{min}}{I_{nom}} \times 100 = \frac{100 - 78}{100} \times 100 \approx 22\%$$

Thus, the circuit exhibits a **22%** current deviation in the saturation region, with a maximum allowable  $V_{OUT}$  of approximately **0.7 V**.

## 1.3 Part 2: Modified Design for Increased Output Impedance (Circuit 1b)

### 1.3.1 Modification and Dimensions

To increase  $R_{OUT}$  without employing a cascode structure, the channel length  $L$  is increased to reduce channel-length modulation. Since  $\lambda \propto 1/L$ , doubling  $L$  approximately doubles  $R_{OUT}$ .

Table 2: Device Dimensions for Circuit 1b

Parameter	PM0 (Reference)	PM1 (Output)
$W$	$1\text{ }\mu\text{m}$	$10\text{ }\mu\text{m}$
$L$	$200\text{ nm}$	$200\text{ nm}$
$W/L$	5	50
$I_{REF}$	$10\text{ }\mu\text{A}$	Target = $100\text{ }\mu\text{A}$

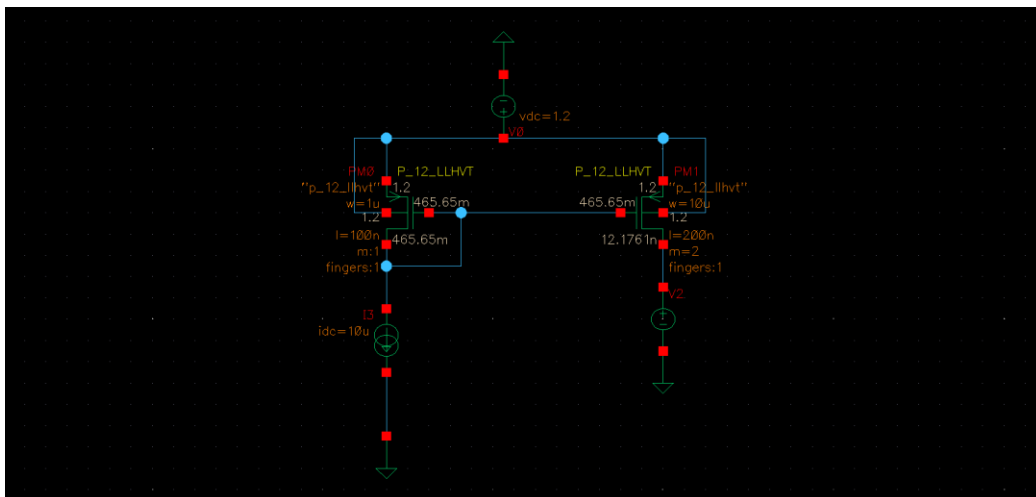


Figure 3: Schematic of the Modified PMOS Current Mirror (Circuit 1b).

### 1.3.2 Simulation Results and Discussion

The DC sweep results are shown in Figure 4.

 


Figure 4: DC Response of Modified PMOS Current Mirror (Circuit 1b). Red:  $|I_{PM1}|$  ( $\mu A$ ), Yellow:  $|R_{OUT}|$  ( $k\Omega$ ).

#### Results:

- $R_{OUT,1b} \approx 48.66 k\Omega$  at  $V_{OUT} = 0.7 V$ .
- Current varies from  $100 \mu A$  to  $88.5 \mu A$ , i.e.  $\approx 11.5\%$  deviation.


**Inference:** Increasing channel length from  $100 nm$  to  $200 nm$  improved output impedance by approximately **40%** and reduced current variation from **22%** to **11.5%**. Hence, the longer channel significantly enhances current source stability without additional biasing overhead.

## 2 Question 2: Low-Voltage Cascode Current Mirror

### 2.1 Problem Statement

Design a low-voltage cascode current mirror capable of sinking  $100 \mu A$  using a  $10 \mu A$  reference current. The circuit should maintain operation for output voltages as low as  $300 mV$  with an additional  $40 mV$  margin for each device's  $V_{DS,sat}$ . The design should include:

- Bias voltage derivation and verification.
- Current versus voltage characteristics.
- Output impedance estimation from both simulation and analytical calculation.

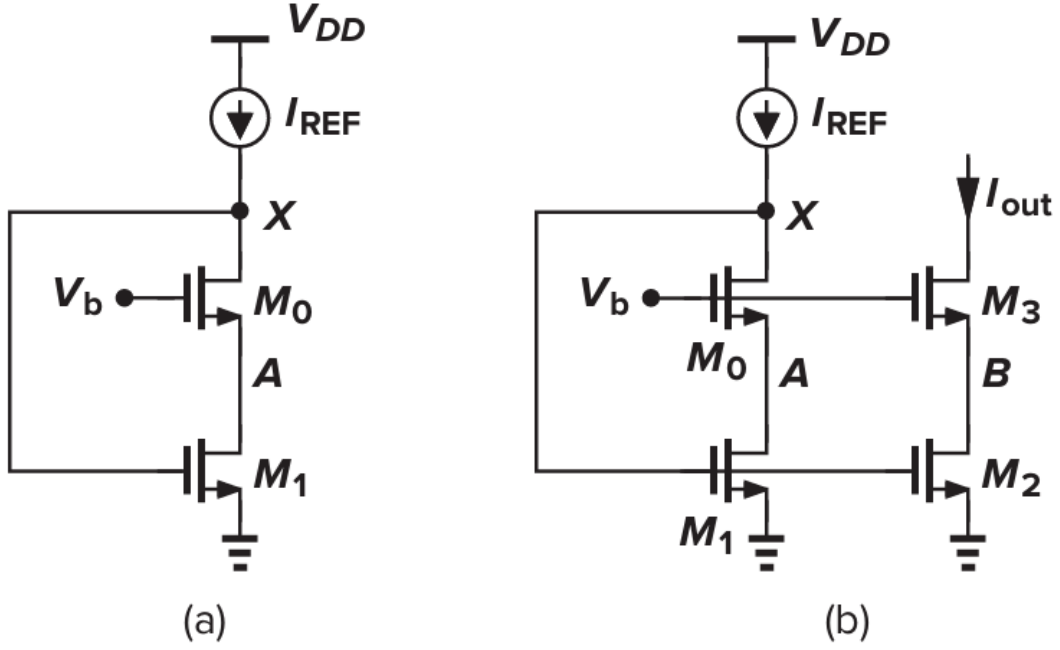

**Figure 5.18** Modification of cascode mirror for low-voltage operation.

Figure 5 : Low-Voltage Cascode Current Mirror Topology.

## 2.2 Bias Voltage and Operating Conditions

For proper biasing, the bias voltage  $V_b$  must satisfy:

$$V_{GS3} + V_{OV} \leq V_b \leq V_{GS1} + V_{th}$$

The simulated sweep (Figure 6) confirms  $V_b = 1\text{ V}$  as the optimal operating point.

 


Figure 6:  $V_b$  choose.

## 2.3 Schematic and Results

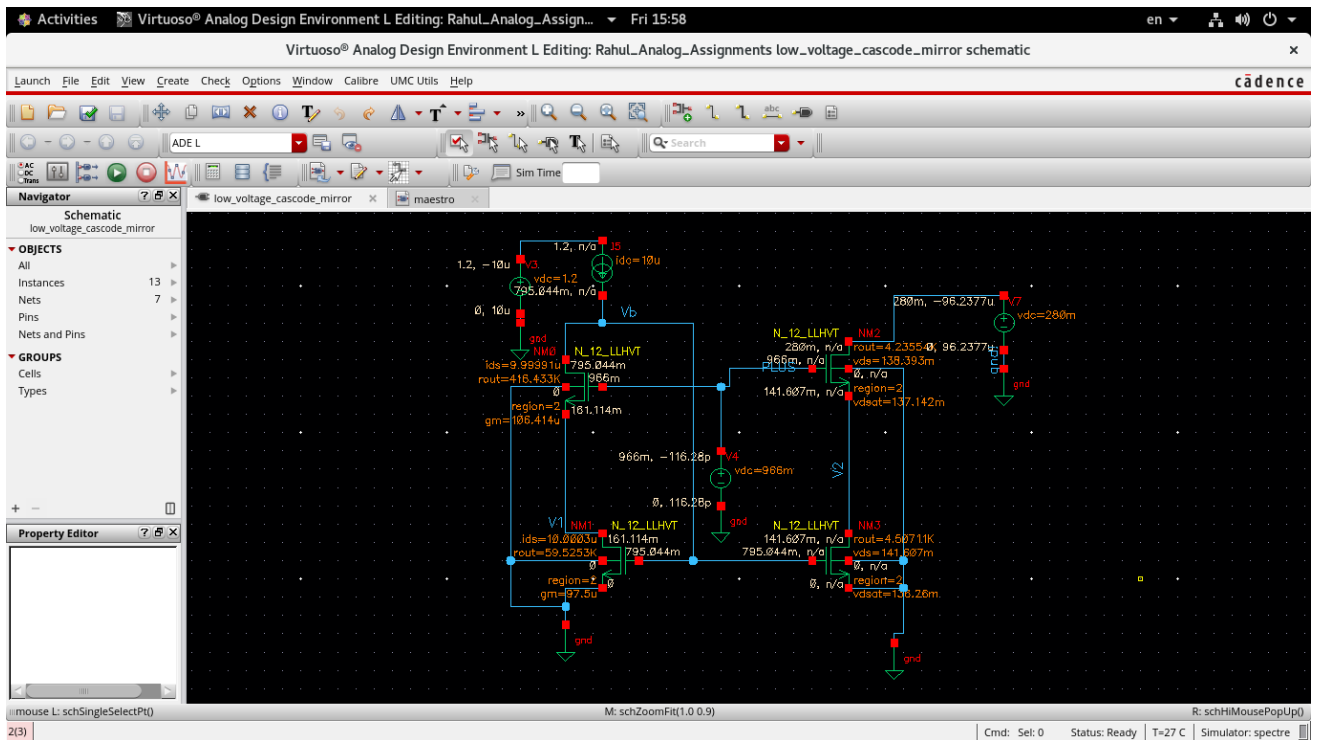


Figure 7: Schematic of the Low-Voltage Cascode Current Mirror.

The DC sweep of  $V_{OUT}$  is shown in Figure 8.

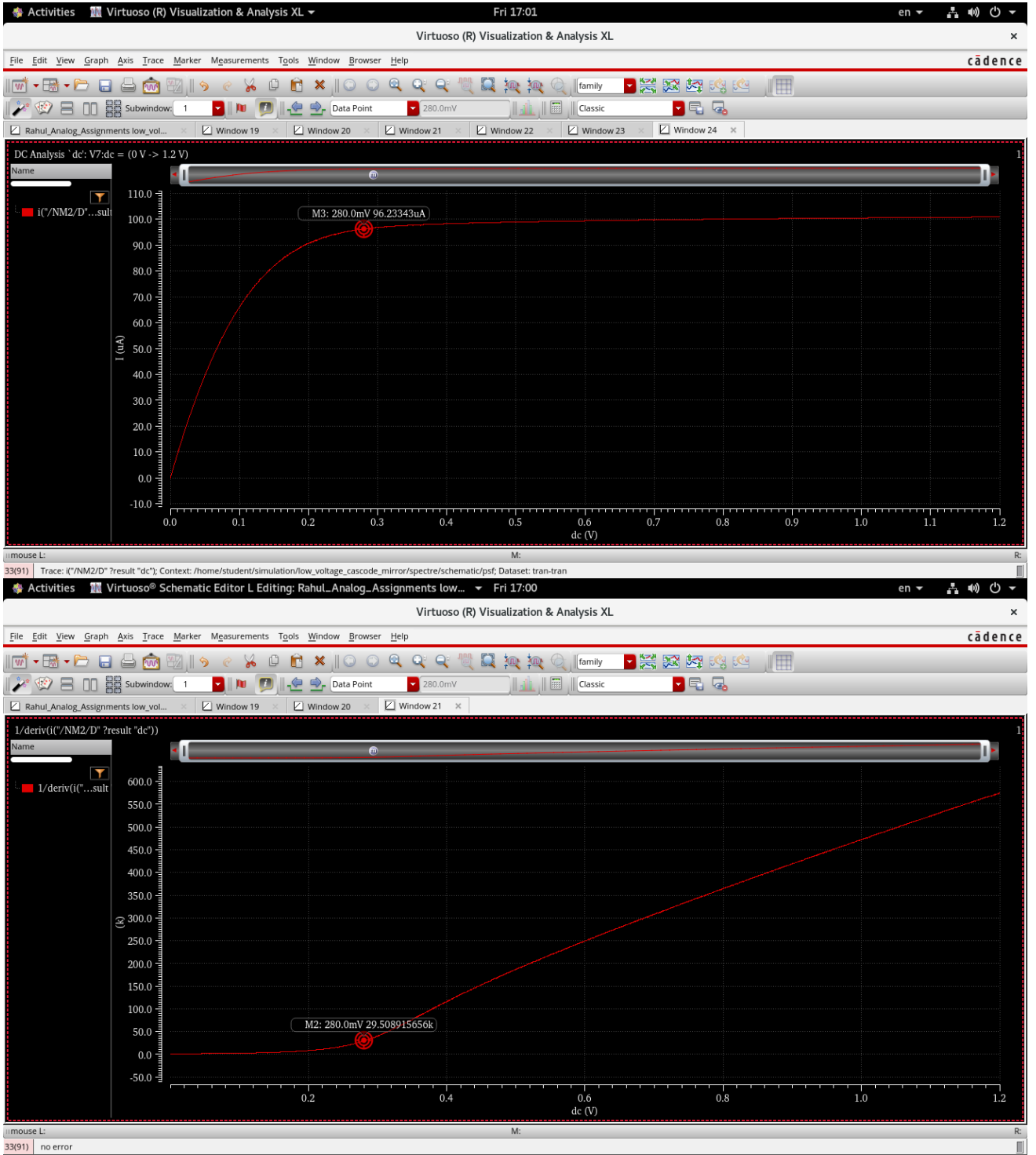


Figure 8: DC Response of Low-Voltage Cascode Current Mirror. First :  $|I_{OUT}|$  ( $\mu A$ ) vs  $V_{out}$ , Second :  $|R_{OUT}|$  ( $k\Omega$ ).

### Key Observations:

- $I_{OUT}$  96.233  $\mu A$  in saturation.
- Minimum output voltage ( $V_{OUT,min}$ ) = 280m V , satisfying low-voltage constraint.
- $R_{OUT,sim}$  29.5089  $k\Omega$  at  $V_{OUT} = 280m V$ .

## 2.4 Analytical Verification of Output Impedance

From DC operating point data:

- $r_{o,NM2} = 4.2355 \text{ k}\Omega$
- $r_{o,NM3} = 4.50711 \text{ k}\Omega$
- $g_{m,NM2} = 911.24 \text{ }\mu\text{S}$

The analytical output impedance at  $V_{out}=280\text{mV}$  is:

$$R_{OUT,calc} \approx r_{o,NM2} + r_{o,NM3} + g_{m,NM2}r_{o,NM2}r_{o,NM3}$$

$$R_{OUT,calc} \approx 26.1380581 \text{ k}\Omega$$

which closely matches the simulated value of  $29.5089 \text{ k}\Omega$ , confirming accurate modeling of small- signal parameters.



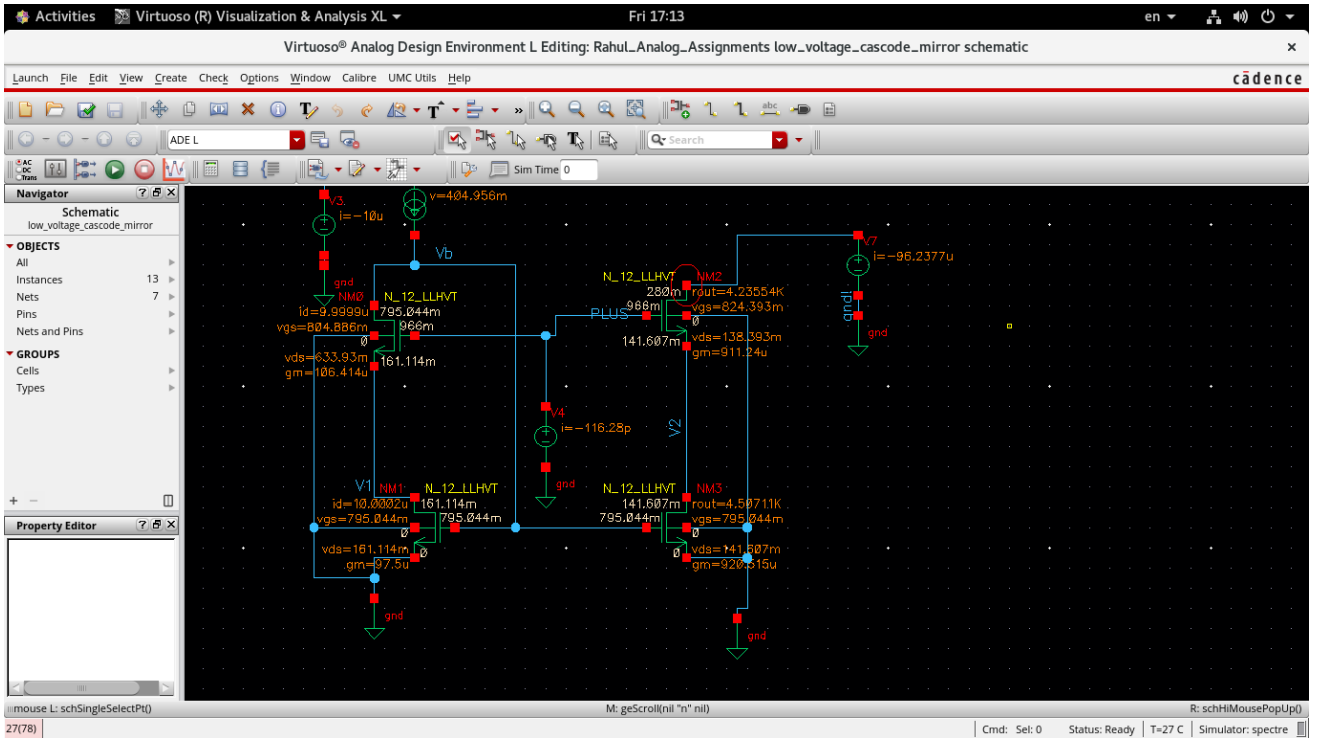


Figure 9: Analytical Verification of  $R_{OUT}$ .

## 2.5 Performance Summary

Table 3: Performance Comparison of Current Mirror Designs

Parameter	Basic PMOS	Modified PMOS	Cascode (NMOS)
$I_{OUT}$ ( $\mu A$ )	100	100	96.2377A
$L$ (nm)	100	200	180
$R_{OUT}$ (k $\Omega$ )	28.75	48.66	20k–575k
Current Variation (%)	22	11.5	$\approx 5$
Topology Type	Simple Mirror	Long-Channel Mirror	Low-V Cascode

## 3 Conclusions and Inference

- Increasing the channel length effectively enhances the output impedance by reducing channel-length modulation, thereby improving current source stability.
- The cascode current mirror significantly improves  $R_{OUT}$  (by  $\sim 4\times$  compared to the basic mirror) while maintaining operation at low voltages.
- The analytical impedance estimation closely agrees with simulation, validating the small-signal model accuracy.
- For analog VLSI applications requiring high precision and low voltage headroom, the low-voltage cascode mirror offers the best trade-off between area, complexity, and performance.

**Final Remark:** This study demonstrates how transistor geometry scaling (particularly  $L$ ) and bias topology optimization directly impact the accuracy, impedance, and voltage headroom

of current mirrors — critical for robust analog circuit design.